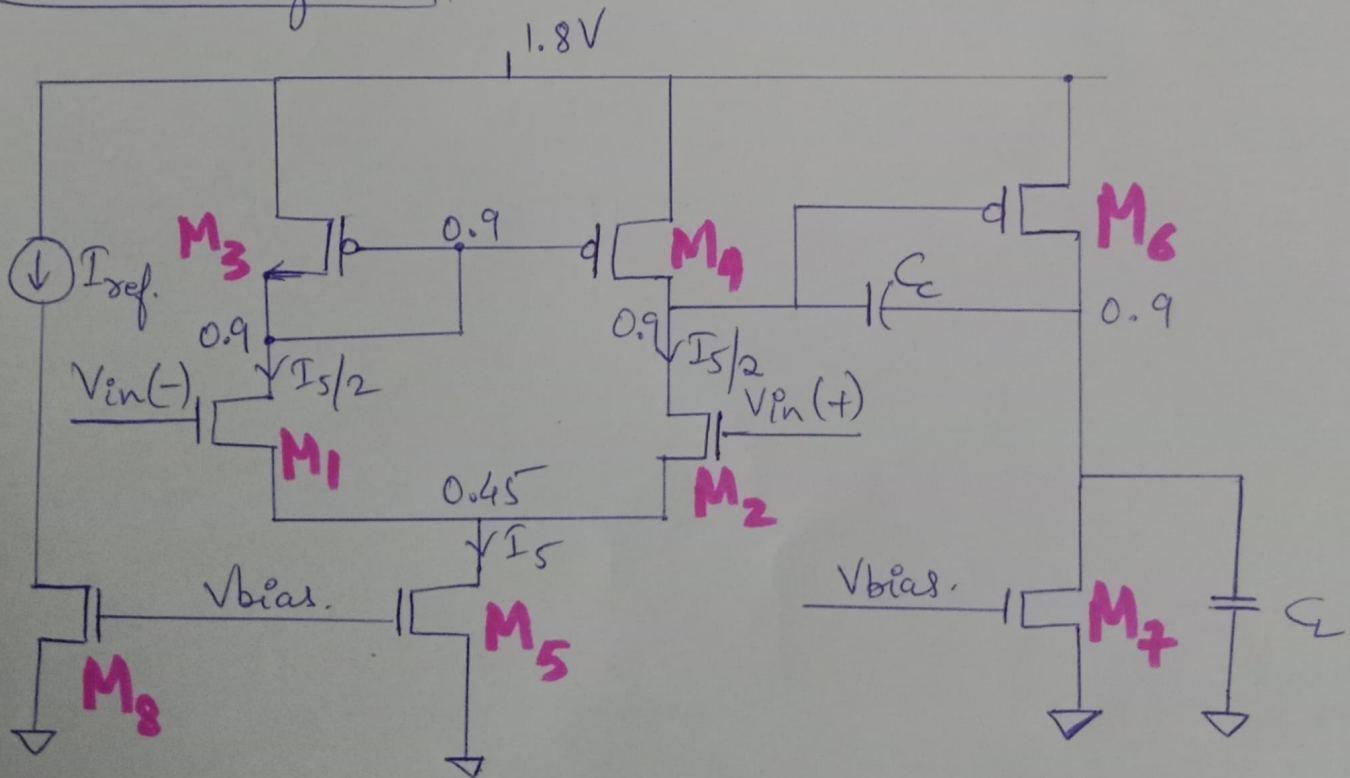


Design for 2 Stage OPAMP

Specification:

- DC Gain = 1000 $\Rightarrow 20 \log_{10} 10^3 = 60 \text{ dB}$
- GBW = 5 MHz
- Process = 180nm Tech
- PM $\geq 60^\circ$
- Slew Rate $\geq 10 \text{ V}/\mu\text{sec}$
- $\text{ICMR}(+) = 1.6 \text{ V}$
- $\text{ICMR}(-) = 0.8 \text{ V}$
- $C_L = 10 \text{ pF}$
- Power dissipation \rightarrow as minimum as possible.
- $V_{DD} = 1.8 \text{ V}$
- $\mu_n C_{ox} = 246.74$ • $\mu_p C_{ox} = 92.75$

Circuit diagram:



Method:-

- $\frac{W}{L}$ ratio of M_3 & M_4 is found using $ICMR(+)$
- $\frac{W}{L}$ ratio of M_1 & M_2 is found using GBW
- I_S is found using SlewRate
- $\frac{W}{L}$ ratio of M_5 is found using $ICMR(-)$
- $\frac{W}{L}$ ratio of M_6 is Gain, design of M_3 & M_4
- M_5 & M_7 are related
- C_c is found using Phase Margin

Calculation:-

C_c for a $PM \geq 60^\circ$
 $\Rightarrow C_c \geq 0.22 C_L$
 $C_c \geq 0.22(10pF)$
 $C_c \geq 2.2pF$
 $C_c \simeq 3pF$

I_S

$$\text{Slew Rate} = \frac{I_S}{C_c}$$

$$I_S = \text{S.R} \times C_c = \frac{10V}{\mu\text{sec}} \times 3pF = \underline{\underline{30\mu A}}$$

For M_1 & M_2

$$g_{m1} = GBW \times C \times 2\pi$$
$$= 5 \times 10^6 \times 3 \times 10^{-12} \times 2\pi$$

$$g_{m1} = 94.24 \mu S$$

WKT

$$\left(\frac{W}{L}\right) = \frac{g_m^2}{\mu_{n\text{ox}} \cdot 2I_D}$$

$$\left(\frac{W}{L}\right)_1 = \frac{(94.24 \mu S)^2}{(246.79 \times 30 \mu)} = \underline{\underline{1.2}}$$

For M_3 & M_4

$$\left(\frac{W}{L}\right)_{3,4} = \frac{2I_{D3}}{\mu_{p\text{ox}} [V_{DD} - I_{CMR(+)} - V_{t3\text{max}} + V_{t1\text{min}}]^2}$$

By simulation we get

$$\underline{V_{t3\text{max}} = 0.433V}$$

$$\underline{V_{t1\text{min}} = 0.31V}$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{30}{92.75 [1.8 - 1.6 - 0.433 + 0.31]^2} = 54.55$$

$$\left(\frac{W}{L}\right)_{3,4} = \underline{\underline{55}}$$

for M₅, M₈

WKT

$$V_{Dsat5} = I_{CMR(-)} - V_{SS} - \sqrt{\frac{I_5}{\beta_1}} - V_{thmax}$$
$$= 0.8 - 1.8 - 0.319 - 0.622 = \underline{\underline{0.100 V}}$$

WKT

$$\left(\frac{W}{L}\right)_5 = \frac{2I_5}{\mu_n C_{ox} \cdot (V_{Dsat5})^2} = \frac{2 \times 30}{246.74 \times (0.100)^2} = 24.31$$

$$\left(\frac{W}{L}\right)_{5,8} \simeq \underline{\underline{24}}$$

for M₆

$$g_{m6} = 10g_{m1} = \underline{\underline{942.4 \mu}}$$

$$g_{m4} = \left[\frac{2I_4 \times \mu_p C_{ox} \times \left(\frac{W}{L}\right)_4}{\cancel{\mu_p C_{ox}}} \right]^{1/2} = \sqrt{(30 \times 92.75 \times 55)}$$

$$g_{m4} \simeq 391.20 \mu$$

$$\left(\frac{W}{L}\right)_6 = \frac{g_{m6} \times \left(\frac{W}{L}\right)_4}{g_{m4}} \simeq 132.49 \simeq \underline{\underline{132}}$$

for M₇

$$I_6 = \frac{\left[\left(\frac{W}{L}\right)_6 \times I_4 \right]}{\left(\frac{W}{L}\right)_4} = \frac{132 \times 15 \mu}{55} = \underline{\underline{36 \mu A}}$$

$$\left(\frac{W}{L}\right)_4 = \frac{I_7 \times \left(\frac{W}{L}\right)_5}{I_5} = \underline{\underline{28}}$$

Data in Cadence / LTSpice!

$$I_{dc} = 30\mu$$

$$C_c = 3pF$$

$$C_L = 10pF$$

for simple calculation keep
 $L = 500n$

$$M_1, M_2 = \begin{cases} W = \del{270u} \del{270u} 600n \\ L = 500n \end{cases}$$

$$M_3, M_4 = \begin{cases} W = 27u \\ L = 500n \end{cases}$$

$$M_5 = \begin{cases} W = 12u \\ L = 500n \end{cases}$$

$$M_6 = \begin{cases} W = 66u \\ L = 500n \end{cases}$$

$$M_7 = \begin{cases} W = 14u \\ L = 500n \end{cases}$$

$$M_8 = \begin{cases} W = 12u \\ L = 500n \end{cases}$$

Analysis:

Total obtained Gain = 63dB
after simulation

Speculated Gain = 60dB

obtained GBW \simeq ~~4.4 MHz~~ 8 MHz

Speculated \simeq 5 MHz

obt PM \simeq 65°

speculated PM \simeq 60°

Power dissipation is minimum.

Result The desired specifications are approximately met.