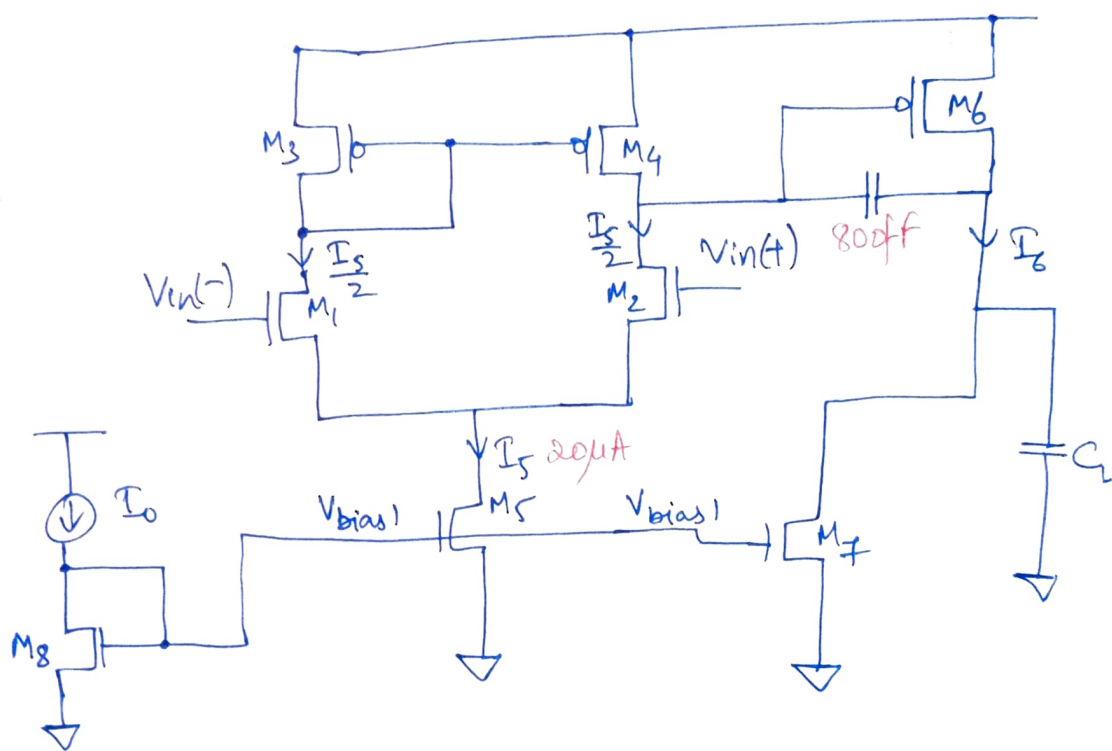


Design for Particular Specification: [180nm Tech]

for

- DC gain = 1000 $\Rightarrow 20 \log_{10} 10^3 = \underline{60dB}$
 - GBW = 30MHz
 - PM $\geq 60^\circ$
 - Slew Rate = 20V/ μ sec
 - ICMR(+) = 1.6V
 - ICMR(-) = 0.8V
 - $C_L = 2pF$
 - Power dissipation $\leq 300\mu W$
 - $V_{DD} = 1.8V$
 - process = 180nm Tech
 - $L_{min} = 180nm$
 - $L \geq 2 \cdot L_{min}$
 - $L = \underline{500nm}$
- To avoid channel length Modulation



$$I_5 = I_0$$

$$m_5 = m_8$$

$\frac{W}{L}$ ratio of M_3, M_4 is found using ICMR(+)

$\frac{W}{L}$ — of M_1, M_2 is found using GBW

~~—~~ I_5 is found using Slewrate

$\frac{W}{L}$ ratio of M_5 is found using ICMR(-)

— of M_6 from Gain & design of M_3 & M_4

M_5 & M_7 are related

C_c is found from Phase Margin!

Design:

• $L = 500\text{nm}$ • $PM \geq 60^\circ$ • $C_c \geq 0.22 C_L$
 $C_c \geq 0.22(2\text{pF})$
 $C_c \geq 0.44\text{pF}$
 $C_c \geq 440\text{fF}$
 $C_c \approx 800\text{fF}$

for I_5

$$\text{slew Rate} = \frac{I_5}{C_c} \Rightarrow \frac{20\text{V}}{\mu\text{s}} \times 800\text{fF} = I_5$$

$$I_5 = 16\mu\text{A} \Rightarrow I_5 \approx 20\mu\text{A}$$

for M_1 & M_2

$$g_{m1} = GB \times C_c \times 2\pi$$

$$g_{m1} = 30\text{MHz} \times 800\text{fF} \times 2\pi$$

$$g_{m1} = 150.79\mu$$

$$g_{m1} \approx 160\mu$$

WKT

$$\left(\frac{W}{L}\right) = \frac{g_m^2}{\mu_{n\text{cox}} 2I_D}$$

$$\left(\frac{W}{L}\right)_1 = \frac{(g_{m1})^2}{\mu_{n\text{cox}} 2I_D} = \frac{(160\mu)^2}{\mu_{n\text{cox}} 2I_D}$$

To derive

$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right) (V_{gs} - V_t)^2$$

$$g_m = \frac{\partial I_D}{\partial V_{gs}} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) \times 2 (V_{gs} - V_t)$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{gs} - V_t)$$

$$g_m^2 = \left[\mu_n C_{ox} \left(\frac{W}{L} \right) \right]^2 \frac{(V_{gs} - V_t)^2}{2} \times 2$$

$$g_m^2 = \frac{2I_D \cdot \mu_n C_{ox}}{1} \left(\frac{W}{L} \right)$$

$$\boxed{\frac{W}{L} = \frac{g_m^2}{\mu_n C_{ox} \cdot 2I_D}}$$

for M_1, M_2 , $2I_D = I_S$

$$I_D = \frac{I_S}{2} = \underline{10 \mu A}$$

$$\left(\frac{W}{L} \right)_1 = \frac{g_{m1}^2}{\mu_n C_{ox} \cdot 2I_D} = \frac{(160 \mu)^2}{30 \times 20 \mu}$$

$$\left(\frac{W}{L} \right)_{1,2} = 4.266 \approx 5$$

$$\boxed{\left(\frac{W}{L} \right)_{1,2} \approx 5}$$

for M_3 & M_4


when we increase V_{in} , M_1 enters triode Region

$$V_{DS} > V_{gs} - V_{t1}$$

$$V_{gs} < V_{D1} + V_{t1}$$

$$V_{in} < V_{D1} + V_{t1}$$
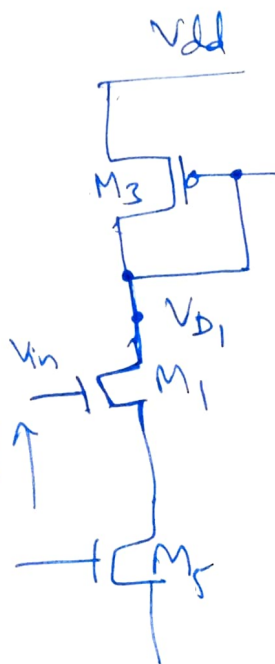
$$V_{inmax} = V_{D1} + V_{t1} \quad \text{--- (1)}$$



$$V_{D1} = V_{DD} - V_{sg3}$$

$$\left[\beta = \mu_n C_{ox} \frac{W}{L} \right]$$

$$V_{D1} = V_{DD} - \left[\sqrt{\frac{2I_3}{\beta_p}} + |V_{t3}| \right]$$

for V_{sg}

$$I_3 = \frac{\mu_{nCox}}{2} \frac{W}{L} (V_{gs} - V_t)^2$$

$$V_{inmax} \leq \underbrace{V_{D1} + V_{t1}}_{min}$$

$$I_3 = \frac{\beta}{2} (V_{gs} - V_t)^2$$

$$ICMR(+) \leq \underbrace{V_{D1}}_{min} + \underbrace{V_{t1}}_{min}$$

$$V_{gs} = \sqrt{\frac{2I_3}{\beta_p}} + |V_{t3}|$$

$$V_{inmax} \leq \underbrace{V_{D1}}_{min} + \underbrace{V_{t1}}_{min}$$

$$\begin{aligned} \mu_{pCox} &= 60 \mu \\ \mu_{nCox} &= 300 \mu \end{aligned}$$

$$ICMR(+) \leq \left[V_{DD} - \left(\sqrt{\frac{2I_3}{\beta}} + |V_{t3}| \right) \right]_{min} + V_{t1min}$$

$$ICMR(+) \leq V_{DD} - \sqrt{\frac{2I_3}{\beta_3}} - |V_{t3}|_{3max} + V_{t1min}$$

$$\frac{2I_3}{\beta_3} = (V_{DD} - ICMR_{max} - |V_{t3}|_{max} + V_{t1min})^2$$

$$\frac{2I_3}{\mu_{pCox} \left(\frac{W}{L} \right)_{34}} = \left[V_{DD} - ICMR_{(+)} - |V_{t3}|_{max} + V_{t1min} \right]^2$$

$$\left(\frac{W}{L} \right)_{34} = \frac{2I_{D3}}{\mu_{pCox} [V_{DD} - ICMR_{(+)} - V_{t3max} + V_{t1min}]^2}$$

By simulation find. $V_{t1min} \approx 470 \text{ mV}$

$$V_{DD} = 1.8$$

$$V_{t3max} \approx 510 \text{ mV}$$

$$V_{D3} = \frac{I_{OS}}{2} = 10 \mu$$

$$\mu_{pCox} = 60 \mu$$

$$ICMR_{(+)} = 1.6 \text{ V}$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{2 \times 10 \mu}{368 \mu [1.8 - 1.6 - 0.51 + 0.47]^2}$$

$$\left(\frac{W}{L}\right)_{3,4} = 13.02$$

$$\boxed{\left(\frac{W}{L}\right)_{3,4} \approx 14}$$

Data in Cadence

$$i_{dc} = 20 \mu$$

$$C_L = 800 f$$

$$M_3, M_8 \begin{cases} W = 3 \mu M \\ L = 500 nM \end{cases}$$

$$M_2, M_1 \begin{cases} W = 7 \mu M \\ L = 500 nM \end{cases}$$

$$M_8, M_9 \begin{cases} W = 6 \mu M \\ L = 500 nM \end{cases}$$

$$M_4 = \begin{cases} W = 87 \mu M \\ L = 500 nM \end{cases}$$

$$M_{10} = \begin{cases} W = 87 \mu M \\ L = 500 nM \end{cases}$$

VCM \rightarrow variable [value initial $\rightarrow 1.6V$] for Higher Range

Analysis:

Results > Point > operating point
(for $I_{CMR} = 0.8V$)
To find gain of 1st Stage $V_{in} = 0.8V$

$$g_{m6}, g_{ds6}, g_{ds1}$$

$$g_{m6} = 143 \mu$$

$$g_{ds6} = 2.17 \mu$$

$$g_{ds1} = 0.9125 \mu \text{ [if small output resistance is high]}$$

To find gain of 2nd Stage

$$g_{m4}, g_{ds4}, g_{ds10}$$

$$g_{m4} = 1.467 m$$

$$g_{ds4} = 7.47 \mu$$

$$g_{ds10} = 43.02 \mu$$

1st stage Gain:

$$V_{CM} = 0.8V$$

$$\frac{1}{r_{o1}} = g_{ds}$$

$$\text{gain} = g_{m6} (r_{o1} \parallel r_{o4})$$

$$= \frac{g_{m6}}{g_{ds6} + g_{ds1}} = \frac{143 \mu}{2.17 \mu + 0.912 \mu} = 46.39$$

$$\text{gain} = 46.36$$

$$\text{gain (indB)} = 20 \log(46.36) = \underline{\underline{33.33 dB}}$$

2nd Stage Gain

$$\text{gain} = \frac{1.467}{7.475 + 43.02}$$

$$\text{gain} = 29.05$$

$$\text{gain (in dB)} = 20 \log 29.05 = 29.26$$

$$\text{total gain} = 33.33 + 29.26 = \underline{\underline{62.59 \text{ dB}}}$$

$$\text{Targeted Gain} = \underline{\underline{60 \text{ dB}}}$$

$$\text{Our Gain} = \underline{\underline{62.59 \text{ dB}}}$$

$$[\text{Gain for } I_{CMR} = 1.6V] \quad V_{in} = 1.6V$$

$$g_{m6} = 158.1 \mu$$

$$g_{ds6} = 5.9 \mu$$

$$g_{ds1} = 1.069 \mu$$

$$g_{m4} = 1.575 \mu$$

$$g_{ds4} = 10.77 \mu$$

$$g_{ds10} = 29.78 \mu$$

$$\text{1st stage Gain} = \frac{158.1}{5.9 + 1} = 22.91 \Rightarrow \underline{\underline{27 \text{ dB}}}$$


$$\text{2nd stage Gain} = \frac{1575}{10.77 + 29.75} = 38.84 \Rightarrow \underline{\underline{31.78 \text{ dB}}}$$

$$\text{Total Gain} = 27 + 31.78 = \underline{\underline{58.98 \text{ dB}}}$$

$$\text{Targeted Gain} = \underline{\underline{60 \text{ dB}}}$$

$$\text{Our Gain} = \underline{\underline{58.98 \text{ dB}}}$$

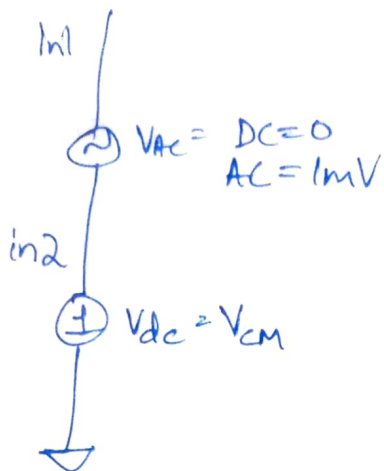Now to increase gain using simulation:-
so introduce an AC source



To plot bodeplot were introducing a small AC source too

AC analysis > frequency >

Start-Stop > start - 100

stop - 100M

Calculate for 800mV

Result > Direct plot > AC Gain & Phase

Simulation Gain = 62.5dB

Our Gain = 62.59dB

BW = 24.17MHz

Phase Margin = 65°

GBW = 30MHz got is 24.17MHz

for 1.6V

Gain = 58.85dB

GBW = 26.45MHz

PM = 64°

To get GBW near to wanted value you can change ζ

Power dissipation:-

$$P = V_{DD} \times (\text{Total current})$$

$$= 1.8 \times [125 + 20]$$

$$P = \underline{\underline{261 \mu W}}$$

125 is through
second stage

To find Power dissipation

Output < Save all < select power signal to output
< All < OK

Run simulation

Tools < Result Browser < dc operating point

$$P = \underline{\underline{273 \mu W}} \quad \} \text{ for } 0.8V$$

for $V = 1.6V$

$$\underline{\underline{P = 273 \mu W}}$$